



I\_clk

I\_rst

I\_wave\_sel

A

Up and down counter; sequential

B

sinusoidal wave; sequential

C

D

triangle; sequential

E

sawtooth; sequential

F

multiplexer; combinatory

G

inversor; combinatory

H

multiplexer (with time change); sequential

I

**O\_wav**